A faded, light-colored circuit diagram of a logic chip is visible in the background. It shows a grid of logic cells with various gates and interconnections, typical of a programmable logic device like an FPGA or ASIC.

# LUT-Oriented Boolean Decomposition for Efficient Arithmetic on FPGAs and ASICs

Danila Gorodetsky and Leonel Sousa

*INESC-ID, Instituto Superior Tecnico, Universidade de Lisboa, Portugal*

## high-level representation

“well-suited”  
algebraic formula

splitting input and  
output operands into  
sub-words of smaller  
bit-width

representation of the  
formula as a  
superposition of  
“simple” arithmetic  
functions

## logic design

Boolean  
representations

properties of  
Boolean functions


Boolean  
representations

Boolean  
minimizations

**Efficient representation of  
arithmetic operation**


$$A \cdot B = R$$
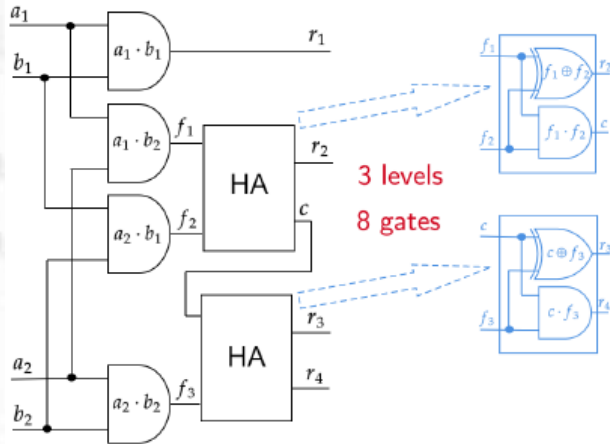
$$A = (a_2, a_1), B = (b_2, b_1), R = (r_4, r_3, r_2, r_1)$$




 a) School-book multiplication

$$\begin{aligned} r_1 &= a_1 \cdot b_1 \\ r_2 &= f_1 \oplus f_2 \\ r_3 &= c \oplus f_3 \\ r_4 &= c \cdot f_3 \\ c &= f_1 \cdot f_2 \\ f_1 &= a_1 \cdot b_2 \\ f_2 &= a_2 \cdot b_1 \\ f_3 &= a_2 \cdot b_2 \end{aligned}$$




3 levels  
8 gates

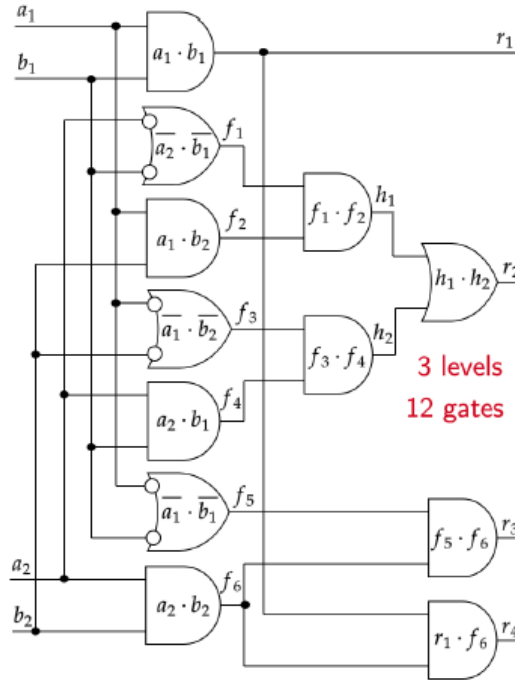

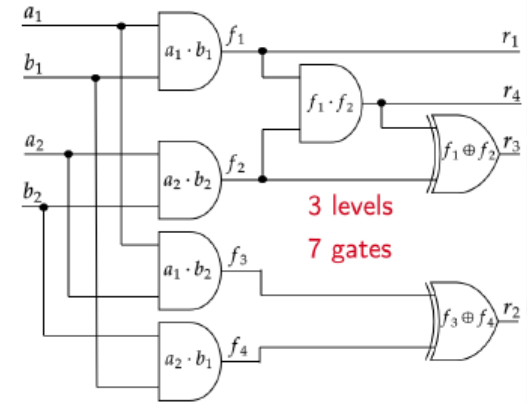b) DNF minimization multiplication

$$\begin{aligned} r_1 &= a_1 \cdot b_1 \\ r_2 &= h_1 \vee h_2 \\ r_3 &= f_5 \cdot f_6 \\ r_4 &= r_1 \cdot f_6 \\ h_1 &= f_1 \cdot f_2, \\ h_2 &= f_3 \cdot f_4 \\ f_1 &= \bar{a}_2 \vee \bar{b}_1 \\ f_2 &= a_1 \cdot b_2 \\ f_3 &= \bar{a}_1 \vee \bar{b}_2 \\ f_4 &= a_2 \cdot b_1 \\ f_5 &= \bar{a}_1 \vee \bar{b}_1 \\ f_6 &= a_2 \cdot b_2 \end{aligned}$$



c) Reed-Muller multiplication

$$\begin{aligned} r_1 &= f_1 \\ r_2 &= f_3 \oplus f_4 \\ r_3 &= r_4 \oplus f_2 \\ r_4 &= f_1 \cdot f_2 \\ f_1 &= a_1 \cdot b_1 \\ f_2 &= a_2 \cdot b_2 \\ f_3 &= a_1 \cdot b_2 \\ f_4 &= a_2 \cdot b_1 \end{aligned}$$

# 6 – stage scalable methodology\*

split operation into partial products of smaller sub-words

## Arithmetic Decomposition

$$F = A_1 \cdot B_1 \cdot C_1 + A_2 \cdot B_2 \cdot C_2 + \dots + A_w \cdot B_w \cdot C_w$$


represent each partial product as a Boolean function  $g_i(X)$

## Boolean Mapping

$$A_1 \cdot B_1 \cdot C_1 = g_1(X_1), A_2 \cdot B_2 \cdot C_2 = g_2(X_2), \dots, A_w \cdot B_w \cdot C_w = g_w(X_w)$$

map minimized functions to FPGA LUTs or ASIC standard cells

## LUT/Library Mapping

 

## Boolean Decompos./Minimiz.


$$F = g_1(h_1(X_1), \dots, h_v(X_v)) \circ g_2(h_1(X_1), \dots, h_v(X_v)) \circ \dots \circ g_w(h_1(X_1), \dots, h_v(X_v))$$

"o" ∈ {+, -, ·}

minimize Boolean functions using Reed-Muller, Karnaugh, or technology-dependent methods

## Adders Tree

ballanced parallel additions

 

combine partial results using balanced parallel addition

## Result Integration

concatenation

$R - P$  if  $R \geq P$   
modular correction  
when required

concatenate sub-results and apply modular correction if  $R \geq P$

- Modular operations (for an arbitrary  $P$ )
  - constant multiplication  $((A \cdot \text{const})(\text{mod } P) = R)^*$
  - modular multiplication  $((A \cdot B)(\text{mod } P) = R)^*, **, *****$
  - modular addition  $((A + B)(\text{mod } P) = S)$
  - modular reduction  $(A(\text{mod } P) = R)^*$
  - Modular division  $((A \cdot x)(\text{mod } P) \equiv 1)$
  - Residue Number System (RNS)
- Standard operations
  - constant multiplication  $(A \cdot \text{const} = R)^{****}$
  - multiplication  $(A \cdot B = R)^{*****}$
  - addition  $(A + B = S)$
  - division by constant  $(A = \text{constant} \cdot Q + \text{residue})^{**}$
  - Miscellaneous operations  $*****: A \cdot B + C, A \cdot B + C \cdot D, \text{ etc.}$
- Floating-point computations
  - multiplication  $(A \cdot B = R)$
  - addition  $(A + B = S)$
  - Normalization
  - Multi-precision computations

\*D. Gorodecky, L. Sousa, "Modular Arithmetic Based on Boolean Functions: A Divide and Conquer Approach" // IEEE Access, Vol. 13, Oct., 2025, pp. 186383-186396.

\*\*D. Gorodecky, L. Sousa, "Scalable architecture of constant division on FPGA" // Proceedings of the 30th IEEE Symposium on Computer Arithmetic, Sep. 4-6, 2023, Portland, Oregon, USA.


\*\*\*D. Gorodecky, L.Sousa, "Two-Operand Modular Multiplication to Small Bit Ranges" // Advanced Boolean Techniques, Springer Nature Switzerland, 2023, p. 111-122.

\*\*\*\*D. Gorodecky, P. Bibilo, "Constant Multiplication Based on Boolean Minimization" // Proceedings of the 14<sup>th</sup> International Workshop on Boolean Problems, Bremen, Germany, Sept. 24-25, 2020.

\*\*\*\*\*D. Gorodecky "Design of Multipliers Using Fourier Transformations" // Further Improvements in the Boolean Domain, Cambridge Scholars Publishing, UK, 2018, Section 3.4, pp. 240-252.

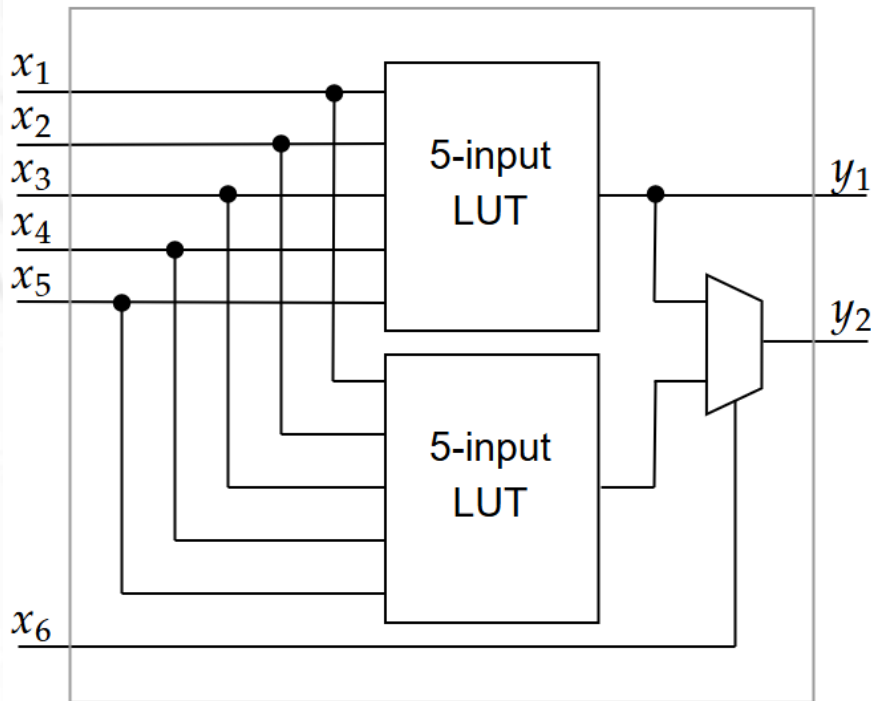\*\*\*\*\*D. Gorodecky, "Two approaches of arithmetic units design" // *it - Information Technology* (De Gruyter), Vol. 66, Issue 4-5, 2025, pp-114-123.





- Decomposition operands to produce small products, where each product represented as Boolean function system (Espresso, ABC)
- $\leq 6$  variables per function: direct mapping to single 6-input LUT
- Functions with  $>6$  variables are decomposed into subfunctions of 5 or 6 variables each
- Architecture-aware exploitation of the Xilinx FPGA LUT structure: 1 LUT = one 6-variables function OR two 5-variables functions

$$y_1(x_1, x_2, \dots, x_5)$$

vs.  $y_1(z_1, z_2, \dots, z_6)$

$$y_2(x_1, x_2, \dots, x_5)$$

$$(A \cdot B) \pmod{3329} = R$$

$$A = (a_{12} a_{11} \dots a_1)$$

$$A_1 = (a_4 a_3 a_2 a_1)$$

$$A_2 = (a_8 a_7 a_6 a_5)$$

$$A_3 = (a_{12} a_{11} a_{10} a_9)$$

$$B = (b_{12} b_{11} \dots b_1)$$

$$B_1 = (b_4 b_3 b_2 b_1)$$

$$B_2 = (b_8 b_7 b_6 b_5)$$

$$B_3 = (b_{12} b_{11} b_{10} b_9)$$

$$A \cdot B = R \pmod{3329} =$$

$$A_1 \cdot B_1 + A_1 \cdot B_2 \cdot 2^4 + A_1 \cdot B_3 \cdot 2^8 +$$

$$A_2 \cdot B_1 \cdot 2^4 + A_2 \cdot B_2 \cdot 2^8 + A_2 \cdot B_2 \cdot 2^{12} +$$

$$A_3 \cdot B_1 \cdot 2^8 + A_3 \cdot B_2 \cdot 2^{12} + A_3 \cdot B_3 \cdot 2^{16} = A_1 \cdot B_1 + A_1 \cdot B_2 \cdot 2^4 + A_1 \cdot B_3 \cdot 2^8 +$$

$$A_2 \cdot B_1 \cdot 2^4 + A_2 \cdot B_2 \cdot 2^8 + A_2 \cdot B_2 \cdot 767 +$$

$$A_3 \cdot B_1 \cdot 2^8 + A_3 \cdot B_2 \cdot 767 + A_3 \cdot B_3 \cdot 2285$$

High – Level Representation

Building blocks:  
8 input Boolean functions

$$A_1 \cdot B_1$$

$$A_1 \cdot B_2 \cdot 2^4$$

$$A_1 \cdot B_3 \cdot 2^8$$

$$A_2 \cdot B_2 \cdot 767$$

$$A_3 \cdot B_3 \cdot 2285$$

$$A \cdot B \pmod{241} = R^*$$

$$A = (a_8 a_7 \dots a_1) \quad B = (b_8 b_7 \dots b_1)$$


$$(A \cdot B) \pmod{241} =$$

$$((a_3 a_2 a_1) \cdot (b_3 b_2 b_1) + (a_3 a_2 a_1) \cdot (b_6 b_5 b_4) \cdot 2^3 + (a_3 a_2 a_1) \cdot (b_8 b_7) \cdot 2^6 +$$

$$(a_6 a_5 a_4) \cdot (b_3 b_2 b_1) \cdot 2^3 + (a_6 a_5 a_4) \cdot (b_6 b_5 b_4) \cdot 2^6 + (a_6 a_5 a_4) \cdot (b_8 b_7) \cdot 30 +$$

$$(a_8 a_7) \cdot (b_3 b_2 b_1) \cdot 2^6 + (a_8 a_7) \cdot (b_6 b_5 b_4) \cdot 30 + (a_8 a_7) \cdot (b_8 b_7) \cdot 240 \pmod{241} =$$

$$R = (r_8 r_7 \dots r_1)$$

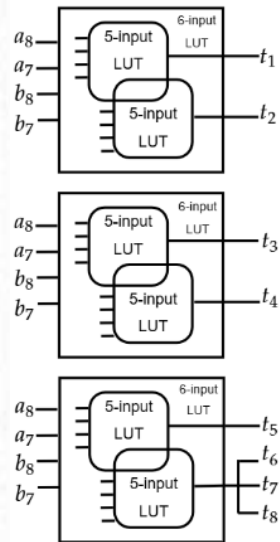

$$t_1 = a_8 \cdot (b_8 \cdot \overline{b_7} \vee \overline{a_7} \cdot b_7) \vee a_7 \cdot b_8 \cdot \overline{b_7} =$$

$$\overline{b_7} \oplus \overline{b_8} \cdot \overline{b_7} \oplus \overline{a_7} \oplus \overline{a_7} \cdot \overline{b_7} \oplus$$

$$a_8 \cdot a_7 \oplus a_8 \cdot a_7 \cdot b_8 \cdot \overline{b_7},$$

$$t_2 = a_8 \cdot b_7 \cdot (\overline{a_7} \vee \overline{b_8}) \vee a_7 \cdot b_8 \cdot (\overline{a_8} \vee \overline{b_7}) =$$

$$a_7 \cdot b_8 \oplus a_8 \cdot b_7,$$

$$t_3 = a_8 \cdot (\overline{b_8} \cdot b_7 \vee \overline{a_7} \cdot b_8 \cdot \overline{b_7}) \vee \overline{a_8} \cdot a_7 \cdot b_8 =$$

$$a_7 \cdot b_8 \oplus a_8 \cdot b_7 \oplus a_8 \cdot b_8 \oplus a_8 \cdot b_8 \cdot b_7,$$

$$t_4 = a_8 \cdot (b_8 \vee b_7) \vee a_7 \cdot b_8 =$$

$$a_7 \cdot b_8 \oplus a_8 \cdot b_7 \oplus a_8 \cdot b_8 \oplus a_8 \cdot b_8 \cdot b_7 \oplus a_8 \cdot a_7 \cdot b_8,$$

$$t_5 = \overline{a_8} \cdot a_7 \cdot \overline{b_8} \cdot b_7 =$$

$$a_7 \cdot b_7 \oplus a_7 \cdot b_8 \cdot b_7 \oplus a_8 \cdot a_7 \cdot b_7 \oplus a_8 \cdot a_7 \cdot b_8 \cdot b_7,$$

$$t_6 = t_7 = t_8 = (a_8 \vee a_7) \cdot (b_8 \vee b_7) =$$

$$1 \oplus \overline{b_8} \cdot \overline{b_7} \oplus \overline{a_8} \cdot \overline{a_7} \oplus \overline{a_8} \cdot \overline{a_7} \cdot \overline{b_8} \cdot \overline{b_7}$$

$$((a_8 a_7) \cdot (b_8 b_7) \cdot 240) \pmod{241} = T(t_8 t_7 \dots t_1)$$

decimal	$(a_8 a_7) \cdot (b_8 b_7) \cdot 240$	$a_8$	$a_7$	$b_8$	$b_7$	$t_8$	$t_7$	$t_6$	$t_5$	$t_4$	$t_3$	$t_2$	$t_1$	decimal $T$
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
240	240	1	0	1	1	1	1	0	0	0	0	0	0	240
239	239	0	1	1	0	1	1	1	0	1	1	1	1	239
238	238	0	1	1	1	1	1	0	1	1	1	0	0	238
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
239	239	1	0	0	1	1	1	1	0	1	1	1	1	239
237	237	1	0	1	0	1	1	1	0	1	1	0	1	237
235	235	1	0	1	1	1	1	0	1	0	1	0	1	235
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0
238	238	1	1	0	1	1	1	0	1	1	0	1	0	238
235	235	1	1	1	0	1	1	1	0	1	0	1	1	235
232	232	1	1	1	1	1	1	0	1	0	0	0	0	232

$$\frac{X}{d} = \{ \mathbf{Quotient}, \mathbf{Residue} \} \quad \delta = \lceil \log_2 d \rceil$$

$$1. \quad X = (X_3 X_2 X_1) = (X_3 \underbrace{00 \dots 0}_{2 \cdot \delta}) + (X_2 \underbrace{00 \dots 0}_{\delta}) + (X_1)$$

Ex.  $d=7, X=489=400+80+9$

$$2. \quad \frac{(X_3 \underbrace{00 \dots 0}_{2 \cdot \delta})}{d} = \{Q_3, R_3\}, \quad \frac{(X_2 \underbrace{00 \dots 0}_{\delta})}{d} = \{Q_2, R_2\}, \quad \frac{X_1}{d} = \{Q_1, R_1\}$$

Ex.  $\frac{400}{7} = \{57, 1\}, \frac{80}{7} = \{11, 3\}, \frac{9}{7} = \{1, 2\}$

$$3. \quad \frac{R_3 + R_2 + R_1}{d} = \{Q_t, R\}, \quad Q_3 + Q_2 + Q_1 + Q_t = Q$$

Ex.  $\frac{1+3+2}{7} = \{0, 6\}, 57+11+1+0=69=Q, R=6$

## Xilinx Vivado 2022.2

```
{xc7k70tfbg484-3 "Kintex-7"}
{xc7a100tcsq324-1 "Artix-7"}
{xc7k50tffg484-3 "KintexUS+"}
```

```
{default_no_clk 0 "Default_NoClock"
```

```
{default_10ns 10 "Default_100MHz"
{default_1ns 1 "Default_1GHz"
{area_no_clk 0 "Area_NoClock"
{area_10ns 10 "Area_100MHz"
{area_1ns 1 "Area_1GHz"
{speed_no_clk 0 "Speed_NoClock"
{speed_10ns 10 "Speed_100MHz"
{speed_1ns 1 "Speed_1GHz"
{area_max 0 "Area_Max_Optimization"
{area_seq 0 "Area_Sequential_Opt"
{speed_5_def 5 "Speed_200MHz_Default"
{speed_5_perf 5 "Speed_200MHz_Performance"
{speed_3_def 3 "Speed_333MHz_Default"
{speed_3_perf 3 "Speed_333MHz_Performance"
{speed_1_def 1 "Speed_1GHz_Default"
{speed_1_perf 1 "Speed_1GHz_Performance"}
```

## Synthesis

```
"Vivado Synthesis Defaults"
```

```
"Vivado Synthesis Defaults"
"Vivado Synthesis Defaults"
"Flow_AreaOptimized_high"
"Flow_AreaOptimized_high"
"Flow_AreaOptimized_high"
"Flow_PerfOptimized_high"
"Flow_PerfOptimized_high"
"Flow_PerfOptimized_high"
"Flow_AreaOptimized_high"
"Flow_AreaOptimized_high"
"Vivado Synthesis Defaults"
"Flow_PerfOptimized_high"
"Vivado Synthesis Defaults"
"Flow_PerfOptimized_high"
"Vivado Synthesis Defaults"
"Flow_PerfOptimized_high"
```

## Implementation

```
"Vivado Implementation Defaults"
```

```
"Vivado Implementation Defaults"
"Vivado Implementation Defaults"
"Vivado Implementation Defaults"
"Vivado Implementation Defaults"
"Vivado Implementation Defaults"
"Performance_Explore"
"Performance_Explore"
"Performance_Explore"
"Area_Explore"
"Area_ExploreSequential"
"Vivado Implementation Defaults"
"Vivado Implementation Defaults"
"Vivado Implementation Defaults"
"Performance_Explore"
"Vivado Implementation Defaults"
"Performance_Explore"
```

## Synopsys 2022, Cadence 2022

2 libraries: **scl45nm (45nm)**, tsmc (28nm)

## Time constraints synthesis:

- none (area optimization)
- 1ns (critical path optimization)
- 10ns (balanced optimization)

## FloPoCo (state-of-the-art)

```
flopoco target=kintex7 IntConstDiv wln=bit_range d=divider arch={0,3} alpha={5,6}
flopoco target=kintex7 IntConstDiv computeQuotient=false wln=input_bit_range
d=modulo arch=3 alpha={5,6}
flopoco target=kintex7 IntConstMult wln=bit_range_input c=constant
```

*constant* · *A*

- 7-bit variable *A* and 29-bit prime  $C = 536870909 = 2^{29} - 3$ , as it titled  $29 \times 7$ ;
- 8-bit variable *A* and 46-bit prime  $C = 70368744177629$ , as it titled  $46 \times 8$ ;
- 9-bit variable *A* and 101-bit prime  $C = 2535301200456458802993406409959$ , as it titled  $101 \times 9$ ;
- 9-bit variable *A* and 157-bit  $C = 2^{157} - 7$ , as it titled  $157 \times 9$ ;
- 10-bit variable *A* and 183-bit  $C = 2^{183} - 1$ , as it titled  $183 \times 10$

Vivado								
Multiplication bits × bits	LUTs				critical path (ns)			
	Vivado	lut_5	lut_6	fpc	Vivado	lut_5	lut_6	fpc
7 × 29	24	17	17	24	8.0	7.4	7.2	7.9
8 × 46	71	46	49	78	9	8.1	8.3	9.2
9 × 101	126	79	85	134	13.8	12.2	12.2	13.1
9 × 157	179	44	49	244	14.7	16.3	15.8	16.1
10 × 183	204	18	18	257	15.9	16.3	17	15.5
Cadence								
Multiplication bits × bits	cells				critical path (ns)			
	Cadence	lut_5	lut_6	fpc	Cadence	lut_5	lut_6	fpc
7 × 29	147	228	161	161	0.8	0.3	0.4	0.6
8 × 46	306	808	792	713	0.9	0.7	0.7	1.2
9 × 101	387	1063	1060	1660	0.9	0.9	0.9	1.7
9 × 157	208	483	464	964	0.8	0.6	0.5	1.4
10 × 183	138	133	133	795	0.4	0.5	0.5	1.2
Synopsys								
Multiplication bits × bits	cells				critical path (ns)			
	Synopsys	lut_5	lut_6	fpc	Synopsys	lut_5	lut_6	fpc
7 × 29	2741	298	312	361	1.0	0.4	0.4	0.9
8 × 46	4753	1074	1051	2502	1.2	0.9	0.7	1.1
9 × 101	10804	1620	1601	5798	1.3	0.9	1.0	1.5
9 × 157	17816	617	599	8184	1.4	0.6	0.5	1.3
10 × 183	23348	246	238	8576	1.4	0.4	0.5	1.4

$$(A \cdot B)(\text{mod } P)$$

Vivado						
P	LUTs			critical path (ns)		
	Vivado	lut_5	lut_6	Vivado	lut_5	lut_6
241	145	128	<b>127</b>	13.6	10.9	<b>10.7</b>
491	162	<b>125</b>	129	13.9	<b>10.5</b>	10.9
997	<b>232</b>	244	245	14.8	<b>13.8</b>	13.9
2011	<b>219</b>	282	277	16.2	14.0	<b>14.3</b>
4051	298	<b>295</b>	310	17.1	<b>14.4</b>	14.9

Cadence						
P	cells			critical path (ns)		
	Cadence	lut_5	lut_6	Cadence	lut_5	lut_6
241	<b>2083</b>	2279	2199	2.7	<b>2.0</b>	2.1
491	<b>2335</b>	2852	2891	3.1	<b>2.2</b>	<b>2.2</b>
997	<b>3288</b>	3624	3512	4.0	<b>2.6</b>	<b>2.6</b>
2011	<b>3613</b>	4225	4094	4.6	2.6	<b>2.3</b>
4051	<b>4518</b>	5322	5355	5.2	<b>2.8</b>	3.0

Synopsys						
P	cells			critical path (ns)		
	Synopsys	lut_5	lut_6	Synopsys	lut_5	lut_6
241	<b>2653</b>	4409	4276	3.0	<b>1.5</b>	<b>1.5</b>
491	<b>3302</b>	5395	5103	3.5	<b>1.5</b>	<b>1.5</b>
997	<b>3912</b>	7739	7156	3.8	<b>1.7</b>	1.8
2011	<b>4705</b>	8603	8131	4.4	<b>1.7</b>	<b>1.7</b>
4051	<b>5748</b>	10447	9875	4.7	<b>1.6</b>	<b>1.6</b>

$$A \pmod{P}$$

Vivado									
bit range of A	P	LUTs				critical path (ns)			
		Vivado	lut_6	fpc_0	fpc_3	Vivado	lut_6	fpc_0	fpc_3
168	241	4419	400	7979	380	25.7	17.2	238.4	16.1
	491	4330	467	12333	508	23.6	18.4	281.4	17.9
	997	4706	599	13198	558	23.6	17.0	298.2	16.6
	2011	4290	534	14847	610	25.9	17.7	308.8	16.5
	4051	4225	484	4691	529	25.3	17.5	263.4	17.3
270	241	10024	509	13847	604	33.6	20.5	382.6	17.2
	491	11088	701	17185	826	33.7	23.1	445.7	17.3
	997	11310	760	15061	905	30.7	22.4	444.9	17.2
	2011	11670	834	10454	1005	34.2	21.9	415.0	18.0
	4051	9926	744	7751	861	33.4	21.5	426.8	18.6

Cadence									
bit range of A	P	cells				critical path (ns)			
		Cadence	lut_6	fpc_0	fpc_3	Cadence	lut_6	fpc_0	fpc_3
168	241	19474	5274	9447	8417	40.2	2.3	2.7	2.7
	491	21041	13299	14722	16519	49.1	2.9	3.2	3.1
	997	31824	14280	14868	16519	58.7	2.8	2.9	3.1
	2011	33253	16388	17588	28828	60.7	2.5	3.4	3.4
	4051	27766	10840	13782	14095	51.3	2.7	3.3	3.0
270	241	164957	8178	14489	14134	210.0	2.6	3.0	2.8
	491	225954	21381	24630	27730	280.0	3.3	3.9	3.7
	997	213834	21801	26337	29756	268.0	3.2	3.7	3.9
	2011	173843	25866	29421	34086	198.0	3.3	4.0	4.1
	4051	197444	16374	22502	24480	248.3	2.9	4.0	4.3

Synopsys									
bit range of A	P	cells				critical path (ns)			
		Synopsys	lut_6	fpc_0	fpc_3	Synopsys	lut_6	fpc_0	fpc_3
168	241	23155	10486	19488	27827	33.8	2.13	2.0	2.0
	491	26315	19275	47380	69012	34.3	2.3	2.1	2.2
	997	28844	18799	49922	68247	35.1	2.1	2.2	2.3
	2011	32367	22717	44571	70130	37.3	2.1	2.3	2.3
	4051	35757	16266	30253	40081	38.4	2.0	2.2	2.2
270	241	36428	15758	32067	42038	56.4	2.3	2.3	2.3
	491	42121	28570	89559	150875	57.6	2.6	2.5	2.5
	997	44700	29113	89706	143962	60.1	2.5	2.4	2.5
	2011	49225	33825	88314	139098	64.8	2.3	2.5	2.6
	4051	52826	24686	51673	65493	68.2	2.2	2.5	2.5

# Results: Division by a Constant

$$\frac{A}{d} = \{Quotient, Residue\}$$

Vivado

bit range of A	d	LUTs					critical path (ns)				
		Vivado	[20]	lut_6	fpc_0	fpc_3	Vivado	[20]	lut_6	fpc_0	fpc_3
16	5	30	51	64	71	59	8.0	8.7	7.7	8.4	9.0
	11	37	52	57	154	59	10.6	8.5	8.6	9.7	9.6
	13	37	70	66	184	63	10.3	8.7	8.1	9.2	9.0
32	5	718	125	123	158	155	15.6	15.8	9.5	12.9	10.7
	11	563	158	165	370	182	15.8	16.4	10.1	14.1	11.5
	23	445	186	187	979	197	14.7	15.3	11.1	18.7	11.7
48	47	1144	394	423	2849	410	18.4	22.8	13.5	29.5	13.7
	113	1382	501	523	4672	408	17.6	19.7	13.4	38.1	14.3
	241	1596	750	575	4713	386	18.4	17.2	13.4	35.5	14.3
64	5	2302	385	460	341	523	21.1	30.4	12.8	22.0	14.7
	11	2039	435	467	955	589	22.1	32.3	12.5	27.0	16.0
	23	1532	493	514	2454	542	19.2	33.0	15.5	35.7	15.3

Cadence

bit range of A	d	cells					critical path (ns)				
		Cadence	[20]	lut_6	fpc_0	fpc_3	Cadence	[20]	lut_6	fpc_0	fpc_3
16	5	762	1281	1131	1110	963	1.1	1.3	1.3	1.3	1.4
	11	1335	1413	1344	3225	1346	1.9	1.4	1.4	2.2	1.7
	13	1403	1097	844	4176	1409	1.8	1.2	1.2	3.2	1.4
32	5	2197	3371	2564	2347	2741	1.3	2.1	1.4	2.9	2.0
	11	3108	4132	3677	6774	3847	4.4	2.1	1.7	5.4	2.3
	23	3999	3840	3520	12277	4053	5.0	2.0	1.4	7.0	2.2
48	47	7284	9806	8336	29449	9781	9.1	2.9	2.1	21.1	3.0
	113	8134	8616	8288	47828	8106	9.6	3.0	2.3	31.2	2.8
	241	9500	7401	7393	36713	6345	9.7	2.5	2.2	20.7	2.8
64	5	5485	1019	7662	4825	9768	2.7	4.2	1.9	6.2	3.2
	11	6033	1131	9361	15324	12553	9.8	3.9	2.2	14.6	3.5
	23	7903	1046	9788	27861	11804	11.2	3.5	2.4	16.8	3.3

Synopsys

bit range of A	d	cells					critical path (ns)				
		Synopsys	[20]	lut_6	fpc_0	fpc_3	Synopsys	[20]	lut_6	fpc_0	fpc_3
16	5	1445	2110	1589	3199	2509	2.2	1.1	1.0	1.1	1.3
	11	1945	2221	1939	9980	2701	2.3	1.1	1.1	1.1	1.5
	13	1929	1927	1250	10861	3010	2.2	1.1	1.0	1.1	1.4
32	5	3040	5003	4189	7752	5768	4.2	2.2	1.2	1.5	1.5
	11	4097	5970	5430	21508	6503	5.0	2.1	1.1	2.2	1.6
	23	4990	6090	5398	36635	7138	5.2	2.1	1.1	2.4	1.7
48	47	9414	12709	12620	80152	15172	8.3	3.0	1.1	3.8	1.9
	113	10315	12212	12038	153050	14748	8.3	2.6	1.1	4.5	2.1
	241	11982	10021	10021	336409	111725	8.5	2.2	1.2	5.1	2.0
64	5	5883	15615	16068	14035	16030	8.8	4.5	1.1	2.9	2.0
	11	8269	17185	17121	38097	17102	9.9	4.3	1.2	4.4	2.1
	23	10251	15780	16090	62043	18741	11.1	4.0	1.2	4.8	2.0

- **«Universal» methodology for arithmetic unit design via Boolean decomposition**
- **up to 85× shorter critical path and up to 28× fewer cells" / "up to 2× shorter critical path and up to 20× fewer LUTs**
- **Cadence gives better results than Synopsys**
- **Up to 2× critical path and up to 20× LUTs (Xilinx Vivado)**
- **Runtime: synthesis time is minutes vs. hours for large input bit-widths, compared with the built-in algorithms of Vivado, Cadence, Synopsys, and FloPoCo**